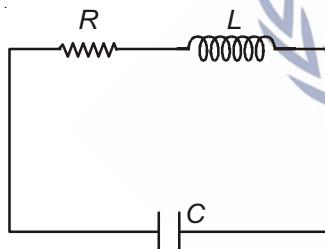


# Alternating Current

1. In a series LCR circuit  $R = 200 \Omega$  and the voltage and the frequency of the main supply is 220 V and 50 Hz respectively. On taking out the capacitance from the circuit the current lags behind the voltage by  $30^\circ$ . On taking out the inductor from the circuit the current leads the voltage by  $30^\circ$ . The power dissipated in the LCR circuit is [AIEEE-2010]


- (1) 242 W      (2) 305 W  
 (3) 210 W      (4) 0 W

2. An LCR circuit is equivalent to a damped pendulum. In an LCR circuit the capacitor is charged to  $Q_0$  and then connected to the  $L$  and  $R$  as shown below :



If a student plots graphs of the square of maximum charge ( $Q_{\text{Max}}^2$ ) on the capacitor with time ( $t$ ) for two different values  $L_1$  and  $L_2$  ( $L_1 > L_2$ ) of  $L$  then which of the following represents this graph correctly? (Plots are schematic and not drawn to scale)

[JEE (Main)-2015]

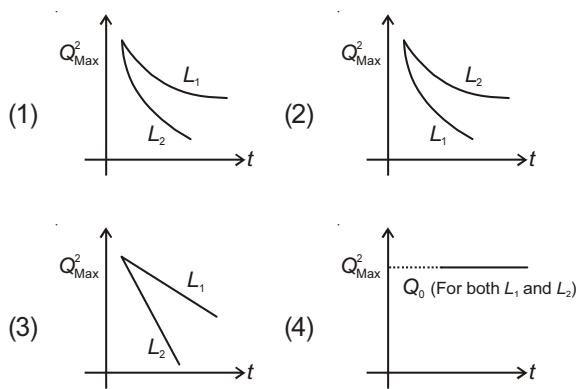

3. An arc lamp requires a direct current of 10 A at 80 V to function. If it is connected to a 220 V (rms), 50 Hz AC supply, the series inductor needed for it to work is close to [JEE (Main)-2016]

- (1) 0.08 H      (2) 0.044 H  
 (3) 0.065 H      (4) 80 H

4. In an a.c. circuit, the instantaneous e.m.f. and current are given by

$$e = 100 \sin 30t$$

$$i = 20 \sin \left( 30t - \frac{\pi}{4} \right)$$

In one cycle of a.c., the average power consumed by the circuit and the wattless current are, respectively [JEE (Main)-2018]

- (1) 50, 10      (2)  $\frac{1000}{\sqrt{2}}, 10$   
 (3)  $\frac{50}{\sqrt{2}}, 0$       (4) 50, 0

5. For an RLC circuit driven with voltage of amplitude

$v_m$  and frequency  $\omega_0 = \frac{1}{\sqrt{LC}}$  the current exhibits resonance. The quality factor,  $Q$  is given by [JEE (Main)-2018]

- (1)  $\frac{\omega_0 L}{R}$       (2)  $\frac{\omega_0 R}{L}$   
 (3)  $\frac{R}{(\omega_0 C)}$       (4)  $\frac{CR}{\omega_0}$


6. A series AC circuit containing an inductor (20 mH), a capacitor (120  $\mu\text{F}$ ) and a resistor (60  $\Omega$ ) is driven by an AC source of 24 V/50 Hz. The energy dissipated in the circuit in 60 s is

- [JEE (Main)-2019]
- (1)  $5.65 \times 10^2 \text{ J}$       (2)  $5.17 \times 10^2 \text{ J}$   
 (3)  $2.26 \times 10^3 \text{ J}$       (4)  $3.39 \times 10^3 \text{ J}$

7. A power transmission line feeds input power at 2300 V to a step down transformer with its primary windings having 4000 turns. The output power is delivered at 230 V by the transformer. If the current in the primary winding of the transformer is 5 A and its efficiency is 90%, the output current would be

[JEE (Main)-2019]

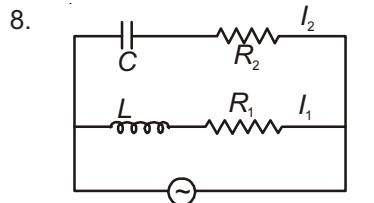- (1) 25 A                         (2) 50 A  
 (3) 45 A                         (4) 35 A



In the above circuit,  $C = \frac{\sqrt{3}}{2} \mu F$ ,  $R_2 = 20 \Omega$ ,

$L = \frac{\sqrt{3}}{10}$  H and  $R_1 = 10 \Omega$ . Current in  $L-R_1$  path is

$I_1$  and in  $C-R_2$  path it is  $I_2$ . The voltage of A.C source is given by

$V = 200\sqrt{2} \sin(100t)$  volts. The phase difference between  $I_1$  and  $I_2$  is

[JEE (Main)-2019]

- (1)  $0^\circ$                          (2)  $60^\circ$   
 (3)  $150^\circ$                          (4)  $90^\circ$

9. An alternating voltage  $v(t) = 220 \sin 100\pi t$  volt is applied to a purely resistive load of  $50 \Omega$ . The time taken for the current to rise from half of the peak value to the peak value is

[JEE (Main)-2019]

- (1) 2.2 ms                         (2) 7.2 ms  
 (3) 5 ms                             (4) 3.3 ms

10. A circuit connected to an ac source of emf  $e = e_0 \sin(100t)$  with  $t$  in seconds, gives a phase

difference of  $\frac{\pi}{4}$  between the emf  $e$  and current  $i$ .

Which of the following circuits will exhibit this?

[JEE (Main)-2019]

- (1)  $RL$  circuit with  $R = 1 \text{ k}\Omega$  and  $L = 10 \text{ mH}$   
 (2)  $RL$  circuit with  $R = 1 \text{ k}\Omega$  and  $L = 1 \text{ mH}$   
 (3)  $RC$  circuit with  $R = 1 \text{ k}\Omega$  and  $C = 10 \mu F$   
 (4)  $RC$  circuit with  $R = 1 \text{ k}\Omega$  and  $C = 1 \mu F$

11. A transformer consisting of 300 turns in the primary and 150 turns in the secondary gives output power of 2.2 kW. If the current in the secondary coil is 10 A, then the input voltage and current in the primary coil are :

[JEE (Main)-2019]

- (1) 440 V and 5 A                 (2) 220 V and 20 A  
 (3) 220 V and 10 A                 (4) 440 V and 20 A

12. A  $LCR$  circuit behaves like a damped harmonic oscillator. Comparing it with a physical spring-mass damped oscillator having damping constant ' $b$ ' the correct equivalence would be

[JEE (Main)-2020]

- (1)  $L \leftrightarrow m, C \leftrightarrow \frac{1}{k}, R \leftrightarrow b$   
 (2)  $L \leftrightarrow k, C \leftrightarrow b, R \leftrightarrow m$

- (3)  $L \leftrightarrow \frac{1}{b}, C \leftrightarrow \frac{1}{m}, R \leftrightarrow \frac{1}{k}$   
 (4)  $L \leftrightarrow m, C \leftrightarrow k, R \leftrightarrow b$

13. In  $LC$  circuit the inductance  $L = 40 \text{ mH}$  and capacitance  $C = 100 \mu F$ . If a voltage  $V(t) = 10 \sin(314t)$  is applied to the circuit, the current in the circuit is given as

[JEE (Main)-2020]

- (1)  $0.52 \sin 314t$                  (2)  $5.2 \cos 314t$   
 (3)  $10 \cos 314t$                      (4)  $0.52 \cos 314t$

14. An inductance coil has a reactance of  $100 \Omega$ . When an AC signal of frequency 1000 Hz is applied to the coil, the applied voltage leads the current by  $45^\circ$ . The self-inductance of the coil is

[JEE (Main)-2020]

- (1)  $6.7 \times 10^{-7} \text{ H}$                  (2)  $5.5 \times 10^{-5} \text{ H}$   
 (3)  $1.1 \times 10^{-1} \text{ H}$                  (4)  $1.1 \times 10^{-2} \text{ H}$

15. A 750 Hz, 20 V (rms) source is connected to a resistance of  $100 \Omega$ , an inductance of  $0.1803 \text{ H}$  and a capacitance of  $10 \mu F$  all in series. The time in which the resistance (heat capacity  $2 \text{ J}/\text{C}$ ) will get heated by  $10^\circ\text{C}$ . (assume no loss of heat to the surroundings) is close to

[JEE (Main)-2020]

- (1) 348 s                             (2) 418 s  
 (3) 245 s                             (4) 365 s

16. An AC circuit has  $R = 100 \Omega$ ,  $C = 2 \mu F$  and  $L = 80 \text{ mH}$ , connected in series. The quality factor of the circuit is

[JEE (Main)-2020]

- (1) 20                                 (2) 2  
 (3) 0.5                                 (4) 400

17. An electrical power line, having a total resistance of  $2 \Omega$ , delivers 1 kW at 220 V. The efficiency of the transmission line is approximately

[JEE (Main)-2020]

- (1) 85%                          (2) 96%  
(3) 72%                           (4) 91%

18. In a series  $LR$  circuit, power of 400 W is dissipated from a source of 250 V, 50 Hz. The power factor of the circuit is 0.8. In order to bring the power factor to unity, a capacitor of value C is added in series to the  $L$  and  $R$ . Taking the value of  $C$  as  $\left(\frac{n}{3\pi}\right)\mu F$ , then value of  $n$  is \_\_\_\_\_.  
[JEE (Main)-2020]

